 



## ECEN 2350: Digital Logic

### Assignment #3

1. [10 points.] Shown below is the pull-down network of a fully complementary CMOS gate.



 - (a) Draw the corresponding pull-up network. In other words, you are given the “bottom half” of a CMOS circuit, and you are to draw the “top half”.
- (b) What is the function performed by the resulting circuit?
2. [8 points.] Draw the truth table for the following circuit. If the output is High-Z, write **Z**.



| $A$ | $B$ | $C$ |
|-----|-----|-----|
| 0   | 0   |     |
| 0   | 1   |     |
| 1   | 0   |     |
| 1   | 1   |     |

3. [10 points.] The power dissipated when a capacitance  $C$  is charged to  $V_{DD}$  and discharged at frequency  $f$  is  $f \cdot C \cdot V_{DD}^2$ . Suppose an inverter drives a load of 50 fF and its input goes up and down at a frequency of 100 MHz. Suppose also that  $V_{DD} = 2$  V. What is the power dissipated by this inverter?
4. [10 points.] Given the circuit described by:  $d = a \cdot b + b \cdot \bar{c}$ , and the logical order of operations (not, and, or):
  - (a) Draw the given circuit using AND, OR, and NOT gates
  - (b) Draw the given circuit using only NAND and and NOT gates
5. [10 points.] Using De Morgan's Law, translate the following into an equation that only uses AND and NOT:  $\overline{x + y \cdot z}$ .  
Show these are equivalent using a truth table.